

4. DC CIRCUIT REGULATION

Circuit regulation means that we change the current / potential difference / electric power on certain elements of the circuit.

Basic knowledge (see summary at the end of the file): Current, voltage, potential, resistance, Ohm's Law. Serial and parallel connection, resultant resistance. Power supplies, electromotive force, internal resistance, terminal voltage. Meters. Kirchhoff's Laws.

NOTATIONS

current: I

electric potential: V or φ ; here φ

voltage: V or U ; here U

electromotive force: ε or E ; here E

terminal voltage: U_t

resistance: R

internal resistance of the source: R_i

internal resistance of the ammeter: R_A

internal resistance of the voltmeter: R_V

total resistance of the potentiometer: R_p

total resistance of the helipot: R_H

variable resistance: R_v or R_1 ; here R_1



A potentiometer is usually used as a variable resistor.

Potentiometer, helipot

A *potentiometer* is a resistor equipped with a third, sliding contact.

It can serve as a *variable resistor* or as a *voltage divider*.

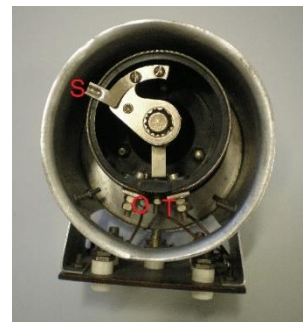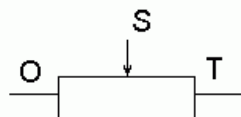In the circuit diagrams, a potentiometer is drawn as:



By moving the sliding contact S from left to right, the resistance R_{OS} between points O and S changes from zero to the maximum resistance of the potentiometer $R_{OT} = R_p$.

This is because $R = (\rho/A) \cdot \ell$, the resistance is proportional to the distance between the contacts, as in this case the resistivity and the cross-sectional area is constant.

4. DC circuit regulation

We will use helical potentiometers – *helipots* – where the wire is wound in the form of a helix.



The position of the sliding contact can be read from a scale.


The resistance R_{OS} is proportional to the scales read n :

$$R_{OS} = \frac{n}{1000} R_H,$$

where

R_H is the resistance of the helipot
(the resistance between points O and T),
and $0 \leq n \leq 1000$.

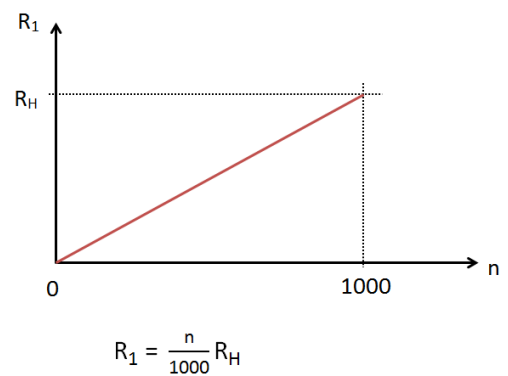Below in the circuit diagrams R_{OS} will be denoted by R_1 .



THEORY

The current or voltage (or power) on a certain element of a circuit can be regulated using a variable resistor. Two typical arrangements are the serial regulation and the potentiometric regulation.

1. Serial regulation

The current (and potential difference and power) on the load with resistance R_L is regulated using a variable resistor connected in series with the resistor.

The loop current

$$I = \frac{E}{R_1 + R_L + R_A + R_i}$$

depends on the value of R_1 (the variable resistance).

Remember that


$$R_1 = \frac{n}{1000} R_H.$$

For $n = 0$, i.e. $R_1 = 0$ we have maximum current:

$$I_{max} = \frac{E}{R_L + R_A + R_i},$$

and for $n = 1000$, i.e. $R_1 = R_H$ the current is minimal:
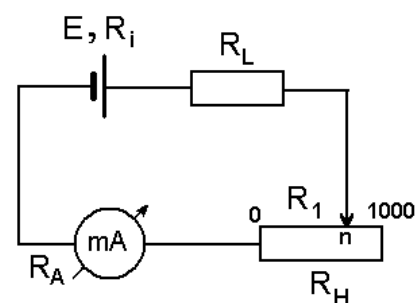
$$I_{min} = \frac{E}{R_H + R_L + R_A + R_i}.$$



2. Potentiometric regulation, voltage divider

The *voltage divider* is often used to regulate the potential difference (and current and power) on an element.

2a. The potentiometer as a voltage divider

Consider the following circuit containing a helipot, a source, and an ideal voltmeter ($R_v = \infty$). Let us derive the formula for the voltage between the sliding contact S and the point O of the helipot in terms of $R_1 = R_{OS}$.

The total resistance in the circuit is $R_t = R_i + R_H$, as no current is flowing across the ideal voltmeter and $R_1 + (R_H - R_1) = R_H$. The current is


$$I = \frac{E}{R_t} = \frac{E}{R_i + R_H} = \text{const.},$$

so the voltage across R_{OS} is

$$U_{OS} = I R_{OS} = \frac{E}{R_i + R_H} R_{OS}.$$

The voltage changes linearly from zero to
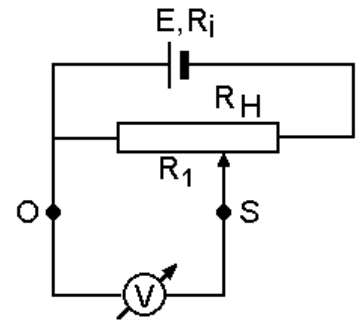
$$U_{\max} = \frac{E}{R_i + R_H} R_H = \frac{R_H}{R_i + R_H} E \quad \text{as the sliding contact S moves from left to right.}$$



2b. Potentiometric regulation of voltage when a loading resistor is applied

Above we have set up a variable-voltage source by means of a helipot, and now we apply this variable voltage to some device.

This device “loads” the source by some resistance R_L .

In this case the total resistance of the circuit is


$$R_t = R_{OS} + (R_H - R_1) + R_i = \frac{R_1 R_L}{R_1 + R_L} + (R_H - R_1) + R_i,$$

the loop current is

$$I^{(L)} = \frac{E}{R_t} = \frac{E}{\frac{R_1 R_L}{R_1 + R_L} + (R_H - R_1) + R_i},$$

and the voltage across R_{OS} is
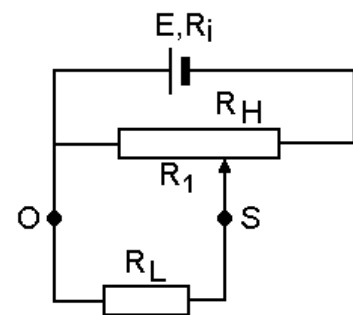
$$U_{OS,(L)} = I R_{OS} = \frac{E}{\frac{R_1 R_L}{R_1 + R_L} + (R_H - R_1) + R_i} \cdot \frac{R_1 R_L}{R_1 + R_L} = \frac{\frac{R_1 R_L}{R_1 + R_L}}{\frac{R_1 R_L}{R_1 + R_L} + (R_H - R_1) + R_i} E.$$




This voltage depends on the position of the sliding contact so that the regulation is

- monotonous (the larger R_1 the larger $U_{OS,(L)}$);
- nearly linear in the vicinity of the two terminals of the potentiometer ($n = 0$ or 1000);
- nearly linear along the whole region if R_L goes to infinity.

(Here $E = 8 \text{ V}$, $R_i = 100 \text{ }\Omega$, $R_H = 2 \text{ k}\Omega$,

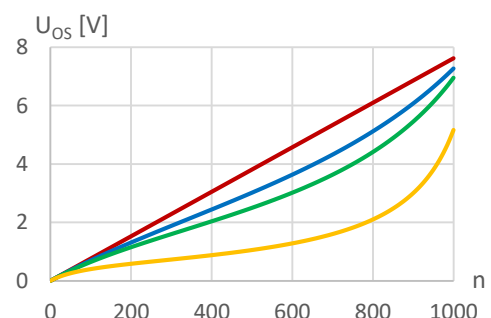— without load; — $R_L = R_H$; — $R_L = 0.5 R_H$; — $R_L = 0.1 R_H$)



REPORT

Introduction:

date of the measurement	name(s) of the student(s)	group no.
4. DC circuit regulation	name of the teacher	

1. Serial regulation

Draw the circuit diagram, and identify the elements of the circuit.

Describe the measurement tasks, what needs to be set and what needs to be read.

What is the purpose of the measurement? What quantities must be determined?

2. Potentiometric regulation


Draw the circuit diagram, and identify the elements of the circuit.

Describe the measurement tasks, what needs to be set and what needs to be read.


What is the purpose of the measurement? What quantities must be determined?

MEASUREMENTS

Tools

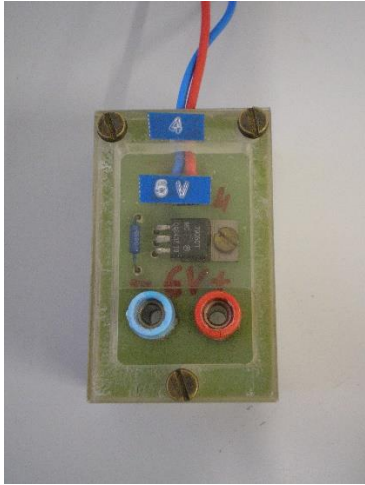

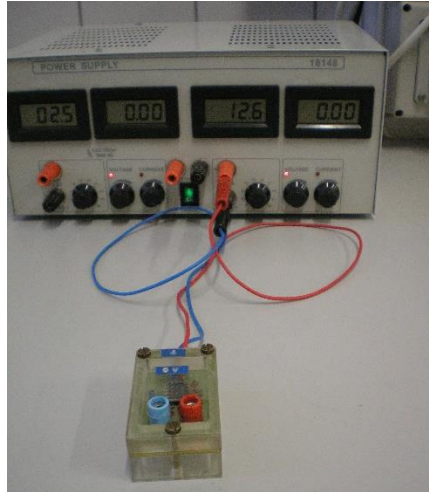
Source.
Nominal voltage: 6 V;
internal resistance: unknown.



The source has to be connected
to the power supply
before the measurement.



Universal digital multimeter

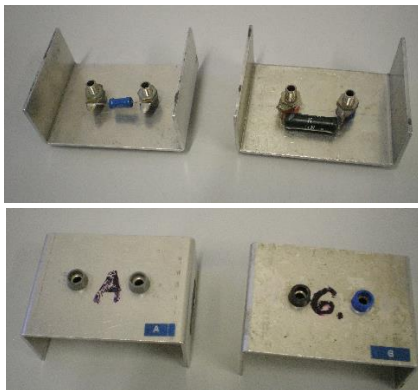

Resistors



Helipot


1. Serial regulation

Tools: source; helipot; resistor denoted by a number; multimeter; connecting wires.

Measure

- the resistance of the “load” R_L denoted by a number,
- the total resistance R_H of the helipot R_H , and
- the terminal voltage U_t of the source.

Set up the serial circuit:

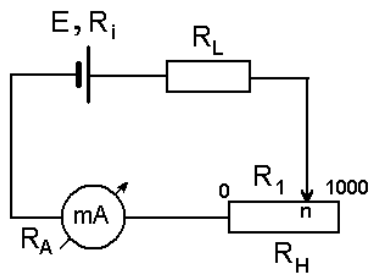

- The helipot is connected with one of the ‘0’ sockets and one of the ‘CS’ sockets.
- The multimeter is connected with the ‘COM’ and the ‘VΩmA°C°F’ sockets.
- Set the multimeter to DC ‘A’ function and choose the ‘20m’ range.

Change the position of the sliding contact from 0 to 1000 scales in 100 scales steps. Measure the current at each scale setting. Collect the measurement data in the table.

EVALUATION

Calculate R_1 using the formula $R_1 = \frac{n}{1000} R_H$.

Optional task: Plot the current I vs. R_1 in SciDAVis and determine the value of the electromotive force E and the sum of the internal resistances $R_A + R_i$ by fitting the function

$$I = \frac{E}{R_1 + R_L + R_A + R_i}$$

The value of R_L is known, it was measured. Pay attention to the units!

Mandatory task: Taking the reciprocal of the current, it is

$$\frac{1}{I} = \frac{1}{E} R_1 + \frac{R_L + R_A + R_i}{E}$$

This is a linear relation between the variable resistance and the reciprocal current.

Plot $1/I$ vs. R_1 (in Excel), calculate the slope and the intercept, then calculate the value of the electromotive force E and the sum of the internal resistances $R_A + R_i$ from the values of the slope and the intercept.

Optional task: Calculate the error interval for E and $R_A + R_i$ based on the standard deviation of the slope and the intercept using the error propagation method.


2. Potentiometric regulation

Tools: source; helipot; resistor denoted by a letter; multimeter; connecting wires.

The internal resistance of the voltmeter is about 50 MΩ, high compared to R_H so it does not appreciably change the current flowing in the circuit

Measure the resistance of the “load” R_L denoted by a letter.

Set up the following circuit:

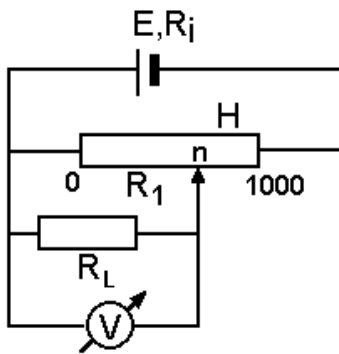

The helipot is connected so that the wires coming from the source are connected to one of the ‘0’ sockets and one of the ‘10k’ (or ‘10000’) sockets; the load and the multimeter are connected to the other ‘0’ socket and one of the ‘CS’ sockets. The multimeter is connected with the ‘COM’ and the ‘VΩmA°C°F’ sockets.

Set the multimeter to DC ‘V’ function and choose the ‘2000m’ or ‘20’ range.

Change the position of the sliding contact and read the voltage at scale divisions as shown in the table. Then disconnect the load R_L and measure the voltage again at n = 300, 600 and 1000. Collect the measurement data in the table.

EVALUATION

Plot U vs. R₁ for both cases, with and without the load.

Without the load it should be a straight line:

$$U = \frac{E}{R_i + R_H} R_1 .$$

Calculate the slope of the line using the least squares method. (Use the formula derived in the curve fitting practice for the slope of y = ax .)

Calculate R_i, the internal resistance of the source, from the slope.

Above, in the serial regulation the sum of R_i+R_A was determined.

Calculate R_A, the internal resistance of the ammeter.


ENTRANCE TEST

Describe the measurements: tools, instructions, quantities measured and calculated, formulas.

Calculations:


1. Calculate the resultant between points

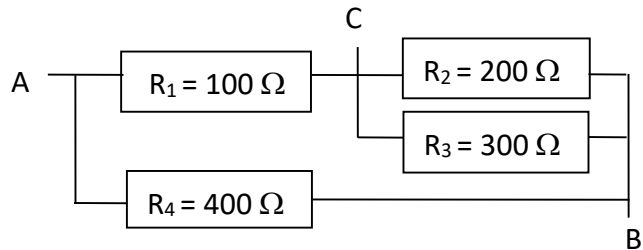- a) A and B;
- b) A and C;
- c) B and C!




Solution:

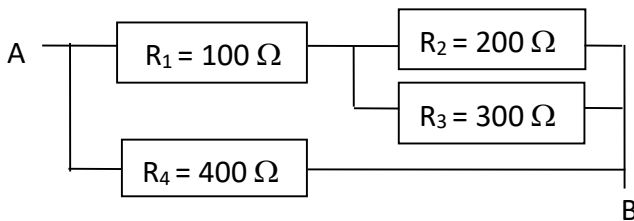a) R_1 is connected in series with the parallel resultant of R_2 and R_3 ; then R_4 is connected in parallel.




$$\frac{200 \cdot 300}{200 + 300} = 120 \, \Omega; \quad 120 + 100 = 220 \, \Omega; \quad R_{AB} = \frac{220 \cdot 400}{220 + 400} = 141.9 \, \Omega.$$

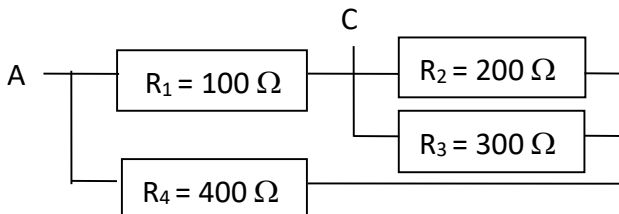b) R_4 is connected in series with the parallel resultant of R_2 and R_3 ; then R_1 is connected in parallel.



$$\frac{200 \cdot 300}{200 + 300} = 120 \, \Omega; \quad 120 + 400 = 520 \, \Omega; \quad R_{AC} = \frac{520 \cdot 100}{520 + 100} = 83.9 \, \Omega.$$

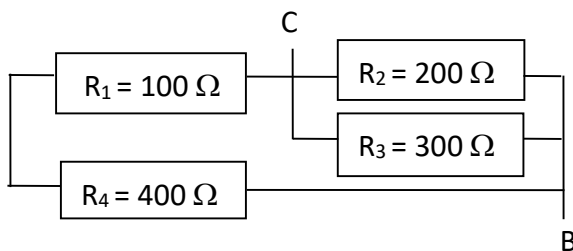c) R_1 and R_4 are connected in series; their resultant is connected in parallel with R_2 and R_3 .




$$\frac{1}{R_{BC}} = \frac{1}{200} + \frac{1}{300} + \frac{1}{400 + 100} \rightarrow R_{BC} = 96.8 \, \Omega.$$

2. The emf of the battery is $E = 10 \text{ V}$, and its internal resistance is 2Ω . $R = 88 \Omega$. M is a digital multimeter.

a) M is used as a voltmeter. In this case its internal resistance is very high compared to R .

What voltage can we read on its display?

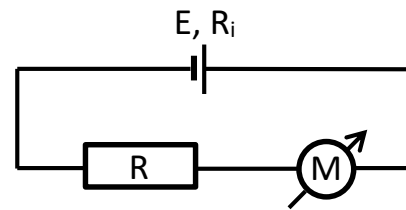b) M is used as an ammeter. We set the 200 mA range where its internal resistance is 10Ω . What current can we read on its display?



Solution:

a) As the resistance of the voltmeter is very high, no current is flowing in the circuit. The voltage across the voltmeter equals the emf E , so we can read 10 V .

b) All resistances are connected in series, the total resistance is $R_t = 2 + 88 + 10 = 100 \Omega$, and the current is $I = E / R_t = 10 \text{ V} / 100 \Omega = 0.1 \text{ A} = 100 \text{ mA}$.

3. We set up a circuit connecting an ideal battery of $E = 12 \text{ V}$ with a constant resistor $R = 100 \Omega$ and a variable resistor R_v in series. $0 \leq R_v \leq 500 \Omega$. Determine the maximum and minimum current and voltage on the constant resistor.

Solution:

The total resistance of the circuit is $R_t = R + R_v = 100 + R_v [\Omega]$.

The current is inversely proportional to R_t : $I = E / R_t$, i.e.

$$I_{\max} = E / R_{t,\min} = E / R = 12 / 100 = 0.12 \text{ A};$$

$$I_{\min} = E / R_{t,\max} = E / (R + R_v) = 12 / (100 + 500) = 0.02 \text{ A}.$$

The voltage across the resistor is proportional to the current: $U_R = I R = E R / R_t$;

$$U_{\max} = I_{\max} R = E = 12 \text{ V};$$

$$U_{\min} = I_{\min} R = E R / (R + R_v) = 12 \cdot 100 / (100 + 500) = 2 \text{ V}.$$


4. The emf of the battery is $E = 10 \text{ V}$, and its internal resistance is negligible. $R_H = 1 \text{ k}\Omega$. The sliding contact is set to $n = 400$ ($n = 0$ is on the left and $n = 1000$ is on the right).

M is a digital multimeter that can be considered as an ideal meter.

What can we read when the multimeter is set as

a) a voltmeter?

b) an ammeter?

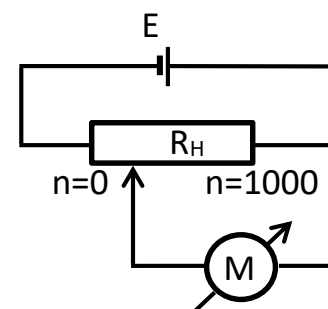

Solution:

a) An ideal voltmeter has infinite internal resistance, no current is flowing through an ideal voltmeter. This means that current only flows through the helipot, and

$$I = E / R_H = 10 \text{ V} / 1000 \Omega = 0.01 \text{ A} = 10 \text{ mA}.$$

The voltmeter is connected to the right part of the helipot that has

$$R_{H,r} = (1000 - 400) / 1000 \cdot R_H = 600 / 1000 \cdot 1000 \Omega = 600 \Omega \text{ resistance, so}$$

$$U = I R_{H,r} = 0.01 \cdot 600 = 6 \text{ V, this voltage can be read on the meter.}$$

b) An ideal ammeter has zero resistance (there is no potential drop on an ideal ammeter). This creates a short cut around the right side of the helipot, i.e. no current is flowing on the right side of the helipot, at the branching point all current goes to the branch of the ammeter. The total resistance of the circuit is the resistance of the left side of the helipot,

$$R_{H,r} = 400/1000 \cdot R_H = 0.4 \cdot 1000 \Omega = 400 \Omega, \text{ so}$$

$$I = E / R_{OC} = 10 \text{ V} / 400 \Omega = 0.025 \text{ A} = 25 \text{ mA}.$$

5. We set up a circuit connecting a battery of $E = 36 \text{ V}$ and unknown internal resistance, a constant resistor $R = 180 \Omega$, a helipot $R_H = 1 \text{ k}\Omega$ as a variable resistor, and an ideal ammeter in series. When the sliding contact of the helipot is set to its middle position the ammeter reads 45 mA .

- Calculate the internal resistance of the battery.
- Calculate the potential drop across the constant resistor for this helipot position.
- Calculate the potential drop across the variable resistor for this helipot position.
- Calculate the terminal voltage of the battery for this helipot position.
- Draw the circuit, including a voltmeter that measures the terminal voltage of the battery.
- Determine the maximum and minimum current in the circuit.
- Calculate the voltage across the constant resistor and the variable resistor, and the terminal voltage of the battery when the current is at maximum.
- Calculate the voltage across the constant resistor and the variable resistor, and the terminal voltage of the battery when the current is at minimum.

Solution:

a) The total resistance of the circuit can be calculated from Ohm's Law written for the whole circuit:

$$R_t = E / I = 36 \text{ V} / 45 \cdot 10^{-3} \text{ A} = 800 \Omega.$$

The resistance of the helipot is $R_H/2 = 0.5 \text{ k}\Omega = 500 \Omega$; $R_A = 0$ (ideal ammeter); so

$$R_t = R_i + R + R_H/2 \quad \rightarrow \quad R_i = R_t - R - R_H/2 = 800 - 180 - 500 = 120 \Omega.$$

b) Applying Ohm's Law for the constant resistor:

$$U_R = I R = 45 \cdot 10^{-3} \text{ A} \cdot 180 \Omega = 8.1 \text{ V}.$$

c) Applying Ohm's Law for the variable resistor:

$$U_{R_V} = I R_V = 45 \cdot 10^{-3} \text{ A} \cdot 500 \Omega = 22.5 \text{ V}.$$

d) The terminal voltage can be calculated in two ways:


- We know that along a closed loop, the sum of all potential differences is zero (Kirchhoff's second law for loops), or, alternatively, the sum of potential drops equals the potential increase, i.e. the voltage across the terminals of the battery:

$$U_t = U_R + U_{R_V} = 8.1 + 22.5 = 30.6 \text{ V}.$$

- The voltage across the terminals of the battery having an internal resistance R_i is less than its electromotive force because of the potential drop on its internal resistance:

$$U_t = E - I R_i = 36 \text{ V} - 45 \cdot 10^{-3} \text{ A} \cdot 120 \Omega = 30.6 \text{ V}$$

e)

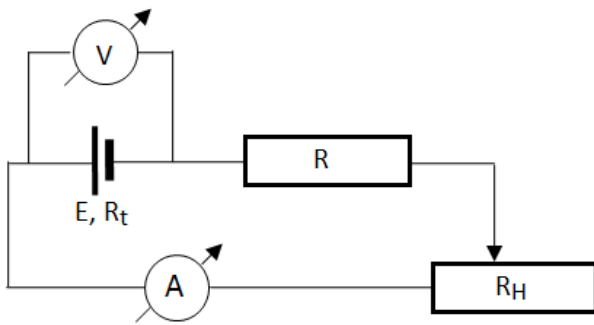

f) $I_{\max} = E / R_{t,\min} = E / (R_i + R + 0) = 36 / (120+180) = 0.12 \text{ A} = 120 \text{ mA};$
 $I_{\min} = E / R_{t,\max} = E / (R_i + R + R_H) = 36 / (120+180+1000) = 0.02769 \text{ A} = 27.69 \text{ mA}.$

g) $I_{\max} = 0.12 \text{ A}:$

$$U_R = 0.12 \cdot 180 = 21.6 \text{ V}$$

$$U_{R_V} = 0.12 \cdot 0 = 0 \text{ V}$$

$$U_t = U_R + U_{R_V} = 21.6 + 0 = 21.6 \text{ V}; \text{ or } U_t = E - I R_i = 36 - 0.12 \cdot 120 = 21.6 \text{ V}.$$

h) $I_{\min} = 0.02769 \text{ A}:$

$$U_R = 0.02769 \cdot 180 = 4.985 \text{ V}$$

$$U_{R_V} = 0.02769 \cdot 1000 = 27.69 \text{ V}$$

$$U_t = U_R + U_{R_V} = 4.985 + 27.69 = 32.68 \text{ V}; \text{ or } U_t = E - I R_i = 36 - 0.02769 \cdot 120 = 32.68 \text{ V}.$$

6. $R_H = 2000 \Omega$; $R = 1200 \Omega$; $E = 4.2 \text{ V}$, the source is ideal ($R_i = 0$).

The sliding contact is set so that the left side of the helipot (parallel to R) has $R_1 = 800 \Omega$.

What does the ideal voltmeter read?

Solution:

R and R_1 are connected in parallel

$$R_p = \frac{1}{\frac{1}{R} + \frac{1}{R_1}} = \frac{1200 \cdot 800}{1200 + 800} = 480 \Omega,$$

then $R_H - R_1 = 2000 - 800 = 1200 \Omega$ is connected in series, the total resistance of the circuit is

$$R_t = R_p + (R_H - R_1) = 480 + 1200 = 1680 \Omega.$$


The current flowing through the source is

$$I = E / R_e = 4.2 \text{ V} / 1680 \Omega = 0.0025 \text{ A} = 2.5 \text{ mA}.$$

The voltmeter is connected in parallel to R but also to R_1 . The resistance between these points is

$R_p = 480 \Omega$, so
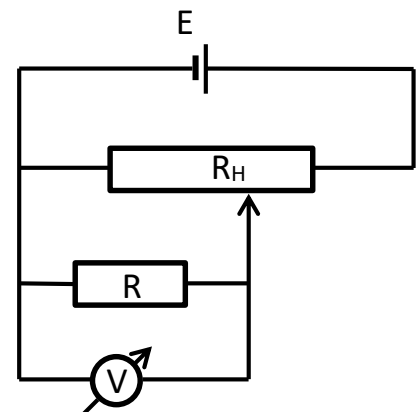
$$U = I R_p = 0.0025 \cdot 480 = 1.2 \text{ V}.$$



BASIC ELECTRICITY**Voltage**

Assume a charge q moves in a static electric field \mathbf{E} from point A to point B. The field exerts the force $\mathbf{F} = q\mathbf{E}$ on the charge and the work done by the field is

$$W_{AB} = \int_A^B \mathbf{F} \cdot d\mathbf{r} = q \int_A^B \mathbf{E} \cdot d\mathbf{r} .$$

The static electric field is conservative, so the work does not depend on the path taken, and the work along a closed loop is zero. The work is determined by the initial and final points of motion A and B and on the charge itself. We define the ratio of work W_{AB} to the charge q as the voltage U_{AB} between points A and B:

$$U_{AB} = \frac{W_{AB}}{q} .$$

The unit of voltage is the Volt (V).

Electric potential

We can assign a scalar property – the electric potential φ – to any point in the field as the work done on unit positive charge when it moves from the given point to the place where this potential is zero. The voltage between the points A and B equal to

$$U_{AB} = \varphi_A - \varphi_B .$$

Electric current

The charged particles – charge carriers – can move freely in conductors, as metals, semiconductors, or electrolytes, but the average of their velocities is zero in the absence of external fields. If there is an electric field in the medium the charge carriers gain a velocity component parallel to the field and the average velocity no longer stays zero. But it does not increase infinitely by the effect of the electric force. The charge carriers will collide with the imperfections of the conductor or with each other and lose their excess velocity gained from the field. As a result, the charge carriers will have a constant average velocity – called *drift velocity* – parallel to the electric field. The stream of charge carriers constitutes a current in the conductor. The intensity of the current is the net charge that flows across the cross section of the conductor in unit time:

$$I = \frac{dq}{dt} .$$

The unit of electric current is the Amper (A)

We speak about stationary current when the current does not change with time. In order to maintain stationary current flowing in a conductor, a stationary electric field must be set up across it. Unlike the static case, there is nonzero electric field in a metal if current flows in it.

Both positive and negative charge carriers contribute to the electric current. The positive charges move in the direction of the field, the negative charges move in the opposite direction.

In a metal, the charge carriers are free electrons. Their drift velocity is proportional to the electric field intensity. In a metal wire, the electric field intensity is constant along the length of the wire, $E = U_{AB}/L$, where L is the length of the piece of wire between points A and B.

Ohm's Law states that the current is proportional to the voltage across a conductor.

The ratio

$$R = \frac{U}{I} \text{ is called resistance.}$$


The unit of resistance is Ohm (Ω).

The resistance of a wire of length L and cross section A is

$$R = \rho \frac{L}{A},$$

where ρ is the resistivity of the material the wire is made of. The unit of resistivity is Ωm .

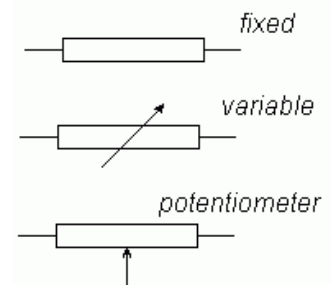Resistors are parts of electric circuits with defined resistance ranging from about 1Ω to several hundred $\text{M}\Omega$. They are made from rods of a poor conductor (carbon grains mixed with insulating resin), or of resistance wire of or a thin strip of metal wound around some insulating support. The symbols for resistors in a circuit diagram are shown in the picture.



The **potentiometer** is a three-terminal device with a sliding contact as the third contact. The resistance between one end and the sliding contact can be varied.

Power

The work of the electric field when a charge dq moves from a place with potential φ_A to a place with potential φ_B is

$$W_{AB} = dq (\varphi_A - \varphi_B) = dq U_{AB}, \text{ where } U_{AB} \text{ is the voltage across A and B.}$$

The power of the electric force is

$$P = \frac{d W_{AB}}{d t} = U_{AB} \frac{d q}{d t} = U_{AB} I .$$

The work would increase the kinetic energy of the electrons in the metal, but they lose this excess KE during collisions. The energy gained from the electric field is transformed to the random motion of the atoms and other electrons of the metal, so it increases the internal energy, so the metal warms up. We call this process *dissipation*. The power dissipated in a resistor is $P = U I$, where I is the current and U is the voltage across the resistor.

The unit of power is watt (W). $1 \text{ W} = 1 \text{ V} \cdot 1 \text{ A}$.

The dissipated power in a resistor can be calculated also as

$$P = U I = I^2 R = U^2 / R .$$

The power used by an electric device – a cooker, heater, a loudspeaker, a motor, a lamp – is defined by the voltage it is connected to and the current that flows through it. This power is transformed to some other kind of energy – heat, sound, mechanical motion, light and so on.

The electric work is measured also in kWh. $1 \text{ kWh} = 1000 \text{ W} \cdot 3600 \text{ s} = 3.6 \cdot 10^6 \text{ J}$.


Sources of electricity: galvanic cells, batteries, generators

There are several means to produce electrical energy from other types of energy.

In a power plant, the generators convert mechanical energy into electric energy. The generators gain their mechanical energy from heat, or from the energy of wind or flowing waters. The commonly used galvanic cells and batteries convert chemical energy into electricity. The solar cells convert light energy – the energy of sunshine into electric energy.

A galvanic cell consists of two electrodes (metals or metal and carbon) immersed into some electrolyte. The ions of metals tend to dissolve in the electrolyte, leaving their outer electrons behind and making this electrode negative with respect to the electrolyte. Different metals dissolve more or less readily so there will be a potential difference between the electrodes. The magnitude of the potential difference between the electrodes of a galvanic cell is called the *electromotive force (emf) E* of the cell. Connecting the electrodes by a metal wire, the electrons accumulated on the negative electrode start to flow toward the positive electrode: we get current in the wire the direction of which is just opposite to the drift velocity of the electrons.

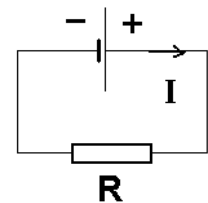To use the electrical energy accumulated in the cell, we connect some load to it: a light bulb, for example. The source and the load connected to it make the simplest electric circuit. The load is represented by a resistor, with resistance R. The electric current flows always from + to – across a resistor.



According to Ohm’s law, the voltage across the resistor is $U = RI$. This voltage usually is lower than the emf of the cell, as the cell itself has got some internal resistance, R_i . As the current flows around, it has to flow across the internal resistance, producing a voltage drop there. So we get Ohm’s law for the whole circuit as

$$E = I (R + R_i) .$$

The voltage across the terminals of a loaded real source is called terminal voltage, U_t :

$$U_t = E - I R_i .$$

(The voltage across the terminals of an ideal voltage source is independent on the load, it is unchanged no matter how big resistance is connected across the terminals.)

Connecting devices in series and in parallel; resultant resistance

Series connection


Two resistors or other devices, elements of the circuit are connected *in series* when they are joined at one end but no other element is connected to their joining point. The free ends of the joined elements are connected into the circuit.

The same current flows through each element in the whole chain as there is no branching point:

$$I_{R1} = I_{R2} = I .$$

The voltages across the resistors add up:

$$U_{AD} = U_{R1} + U_{R2} .$$

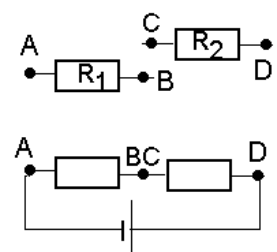

4. DC circuit regulation

The chain of resistors between A and D can be replaced by a single one with a resistance equal to the series resultant R_s of the individual resistances. This series resultant can be calculated knowing that the voltages add up and the same current flows through both resistors, so

$$U_{AD} = U_{R1} + U_{R2} \rightarrow I R_s = I R_1 + I R_2 \rightarrow R_s = R_1 + R_2$$

Parallel connection

Two resistors or other devices are connected in parallel if they are joined at both ends and there is no other element on the connecting wires.

The voltage is the same across both resistors as it is the difference between the potentials of that of the connecting wires:

$$U_{R1} = U_{R2} = U_{AB} .$$


The current flowing through the branches adds up:

$$I_{AB} = I_{R1} + I_{R2} .$$

The joined resistors can be replaced by a single one with a resistance equal to the parallel resultant R_p . The current through this resultant equals the current flowing out from and back into the source. This means that the sum of the current intensities flowing through both resistors is equal to the current flowing through the source.

Combining the additivity of currents with Ohm's law, we get the resultant resistance:

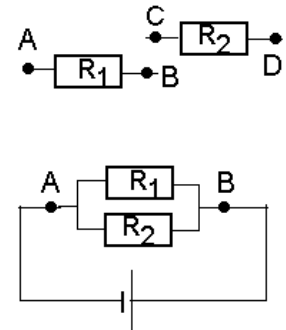
$$I_{AB} = I_{R1} + I_{R2} \rightarrow \frac{U_{AB}}{R_p} = \frac{U_{AB}}{R_1} + \frac{U_{AB}}{R_2} \rightarrow \frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} .$$



Electrical circuits

A more complicated *electrical circuit* can contain several sources and resistors and other devices, all connected with metal wires or strips. We will neglect the resistance of the connecting wires with respect to the other resistances in the circuit.

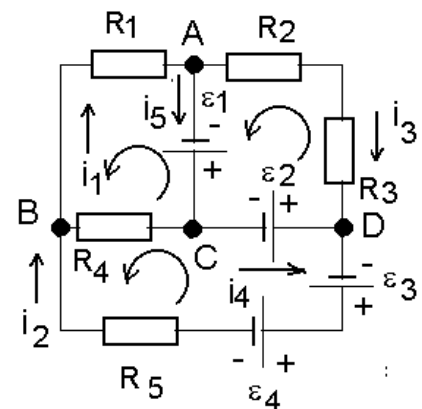A circuit can contain several *loops*: these are non-crossing closed paths. There are *junctions (nodes)* like A, B, C, D, where several wires join. The part of the circuit between two neighbouring junction is called *branch*. In a branch, the same current flows through each element.



Kirchhoff's Laws in electrical circuits

Kirchhoff's first law for junctions

As the electric charge is conserved, and the charge cannot accumulate at a junction, the sum of the currents entering any junction must be equal to the sum of the currents leaving the junction. Using positive sign with the entering current and negative sign with the leaving currents, the net current at a junction must be zero.

Kirchhoff's second law for loops


The electric force is conservative in a static or stationary electric field, the work of the field along a closed path is zero. The same holds for a DC electric circuit. It is possible to assign a potential value (ϕ) to each point of a circuit and the work done by the electric field on a positive unit charge when it moves from point A to B is equal to the difference of the potentials $\phi_A - \phi_B$. Along a closed loop, the sum of all potential differences is zero.

Connecting meters into the circuit

Voltmeters measure voltage across two points of a circuit, so they are connected in parallel to the points where we want to know the voltage.

Ammeters measure current in a branch of the circuit, so they are connected in series with the elements where we want to know the current (we have to break the circuit to insert the ammeter).

Ideal voltmeters have infinite resistance, ideal ammeters have zero resistance, but no meters are ideal so the current and voltage they measure will differ somewhat from the ones without the meter. To calculate the effect of the meter to currents and voltages in the circuit we replace the meter by its internal resistance in the circuit-diagram. The voltmeter reading then is equal to the voltage across its internal resistance. The reading of the ammeter is equal to the current flowing through its internal resistance.

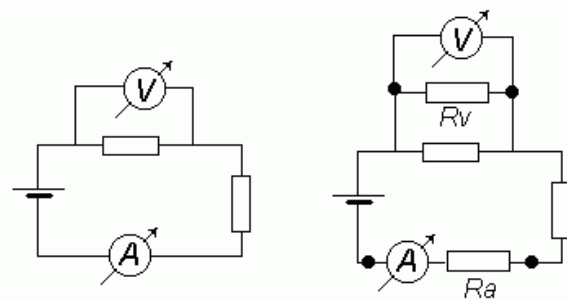

Measuring voltage with a potentiometer: the “ideal voltmeter”

The emf of a source was defined as the voltage across the terminals when nothing is connected to them. But if we want to know the emf the voltmeter has to be connected, and the voltmeter has got some finite resistance. Therefore it will draw current from the source, that current flows through the internal resistance of the source and causes a potential drop across it. The voltmeter will measure less voltage than the emf. How can we measure real emf, without loading the source? Consider a single-loop circuit containing two batteries connected with opposite polarities. The current in the circuit will be proportional to the difference of the emf's of both sources:

$$I = (\epsilon_1 - \epsilon_2) / R ;$$

and no current will flow if the two emf's are equal.

If we had a source the emf of which could be controlled, and we connected it against an unknown battery, we could change the emf till the current in the loop becomes zero. In this case we would know that the unknown emf is equal to the controlled one.

How can we produce a variable-emf voltage source?

We have learnt about how to regulate voltage with a potentiometer, and found out that the voltage across the zero and the sliding contact was proportional to the resistance between zero and the slide if nothing was connected between them:

$$U_{OS} = R / (R_i + R_H) \cdot \epsilon .$$

This voltage can be controlled by moving the sliding contact.

Now we use this potentiometer circuit as a voltage source connected against a battery of unknown emf as shown in the following figure.

G is a very sensitive current-meter, called *galvanometer*, which is able to detect even microamperes, but it is used here to indicate zero-current condition only.

If the galvanometer reads zero current, the variable voltage U_{OS} and the unknown emf, ϵ_x are equal.

$$\epsilon_x = I_p R = I_p (n_x / 1000) R_H ,$$

where the position of the sliding contact is indicated by n_x scales.

Usually we do not know I_p because we do not know ϵ (the emf in the potentiometer circuit) precisely. However, I_p does not depend on the emf measured when zero current is set.

We can replace the unknown battery ϵ_x with a known emf source ϵ_0 . Such are the so-called normal cells, like the Weston cell. (It is a cadmium-mercury cell, with very stable emf of $\epsilon_0 = 1.01865$ V at room temperature.) Again, if the galvanometer reads zero current,

$$\epsilon_0 = I_p R = I_p (n_0 / 1000) R_H .$$

The ratio of both emf-s is

$$\epsilon_x / \epsilon_0 = n_x / n_0 .$$

So by performing two measurements, one with the unknown and one with the known emf source, setting zero current by moving the sliding contact of the potentiometer and reading its position, the unknown emf can be calculated as

$$\epsilon_x = \epsilon_0 \cdot n_x / n_0 .$$

