

NAME, GROUP:

DATE:

working with:

RLC CIRCUIT

1. Resonance curve

Approximate resonant frequency: Hz
here $U_{\text{gen}} = \dots\dots\dots$ V $I = \dots\dots\dots$ mA

Constant voltage $U_{\text{LRC}} = \dots\dots\dots$ V

f (Hz)	I (mA)

f (Hz)	I (mA)

$I_{\text{max}} = \dots\dots\dots$ mA

Resonant frequency: $f_0 = \dots\dots\dots$ Hz

$I_{\text{max}} / \sqrt{2} = \dots\dots\dots$ mA

Frequencies where $I = I_{\text{max}} / \sqrt{2}$: $f_1 = \dots\dots\dots$ Hz $f_2 = \dots\dots\dots$ Hz

2. Vector diagrams

f (Hz)	U_{LRC} (V)	I (mA)	U_{LR} (V)	I (mA)	U_{C} (V)	I (mA)
$0.9 f_0 =$						
$f_0 =$						
$1.1 f_0 =$						

RESULTS

1. Resonance curve

Resistance of the coil: $R = \dots\dots\dots$

Quality factor: $Q = f_0 / (f_2 - f_1) = \dots\dots\dots$

2. Vector diagrams

Frequency: $f = \dots\dots\dots$

Angular frequency: $\omega = \dots\dots\dots$

Capacitance of the capacitor: $C = \dots\dots\dots$

Inductance of the coil: $L = \dots\dots\dots$

From the Thomson's formula $f_0 = \dots\dots\dots$

Quality factor $Q = \frac{1}{R} \sqrt{\frac{L}{C}} = \dots\dots\dots$